


AHP -4

-Achyuth SS

-PES1UG21EC010

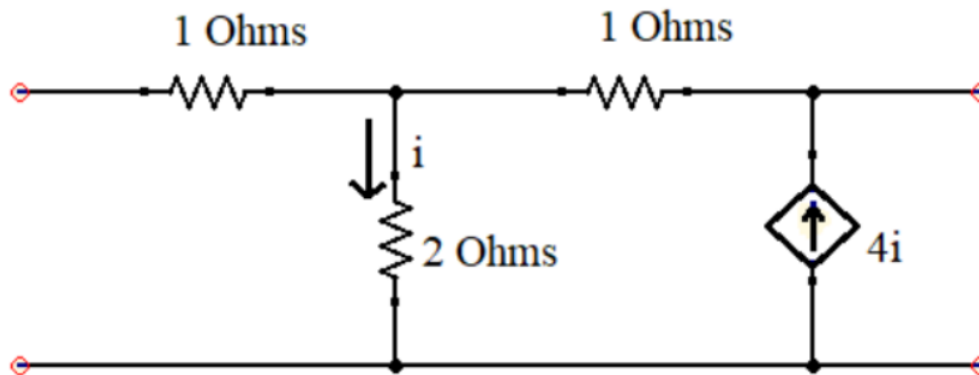1. For the Two-port network given below perform the following. Only employ open circuit or short circuit Analysis
 - a. Find the z-parameters
 - b. Find the y-parameters
 - c. Find the h-parameters
 - d. Find the t-parameters

Verify your results by simulating on QUCS. Simulations are performed using DC sources & probes.



Soln:

Manual solution:

a. z-parameters

For z-parameters

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

when $I_2 = 0$,

z_{11}	$V_1 / I_1 = 1/3 = 0.333\Omega$
z_{21}	$V_2 = -6/3 = -2\Omega$


when $I_1 = 0$:

z_{12}	$V_1 / I_2 = 0.667\Omega$
z_{22}	$V_2 / I_2 = -1\Omega$


or

$$Z = \begin{bmatrix} 0.33 & 0.66 \\ -2 & -1 \end{bmatrix}$$


b. h-parameter

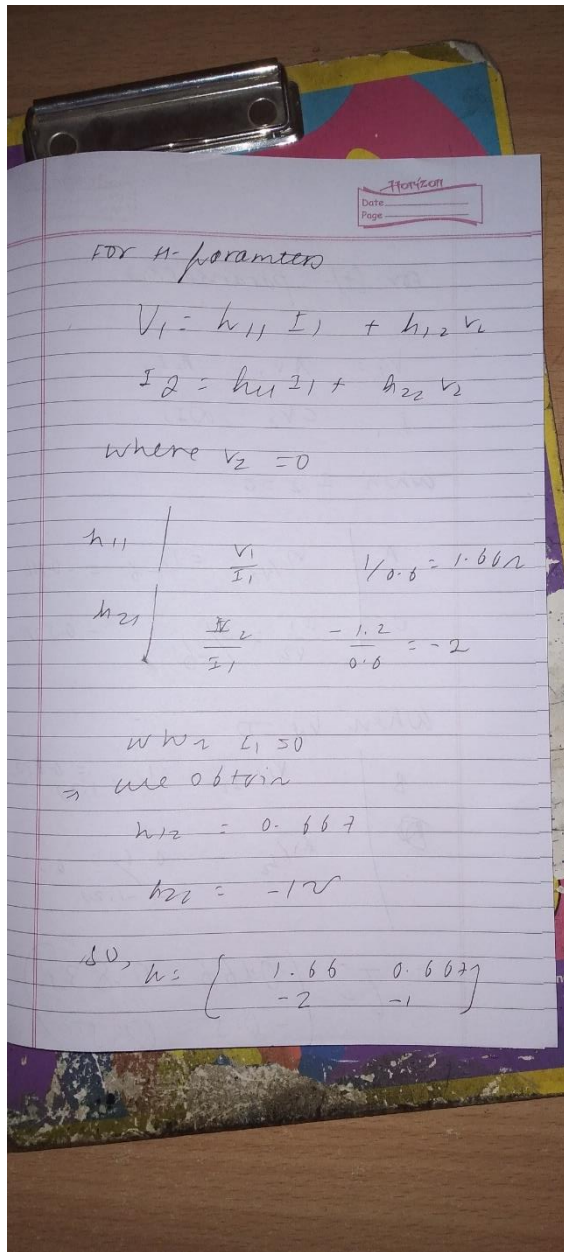

c. T-parameters

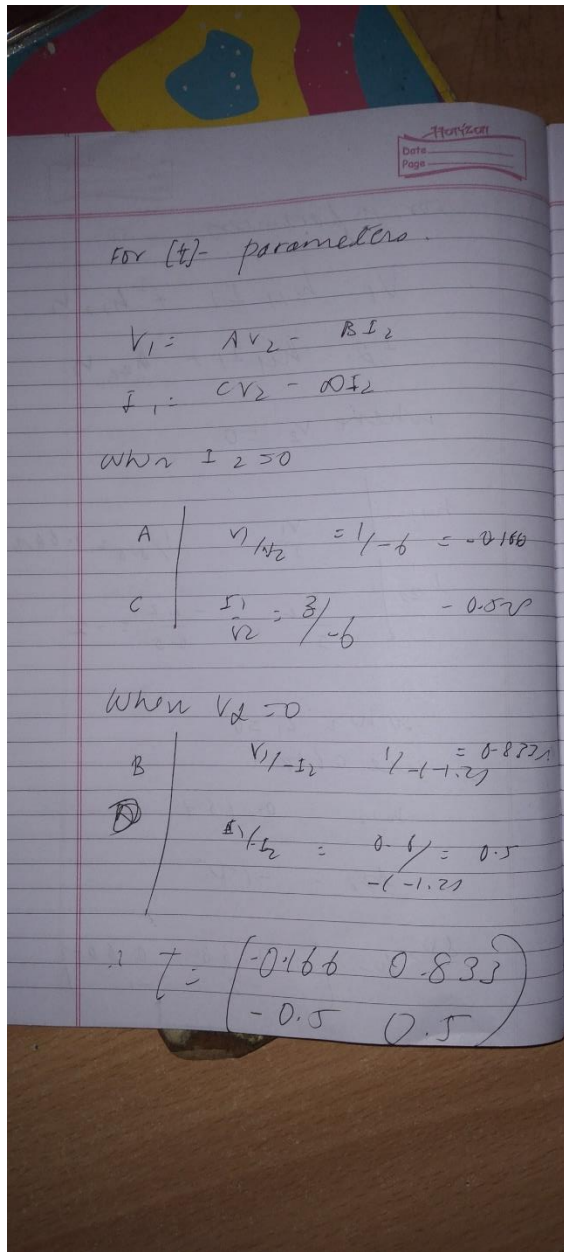


d. y-parameters

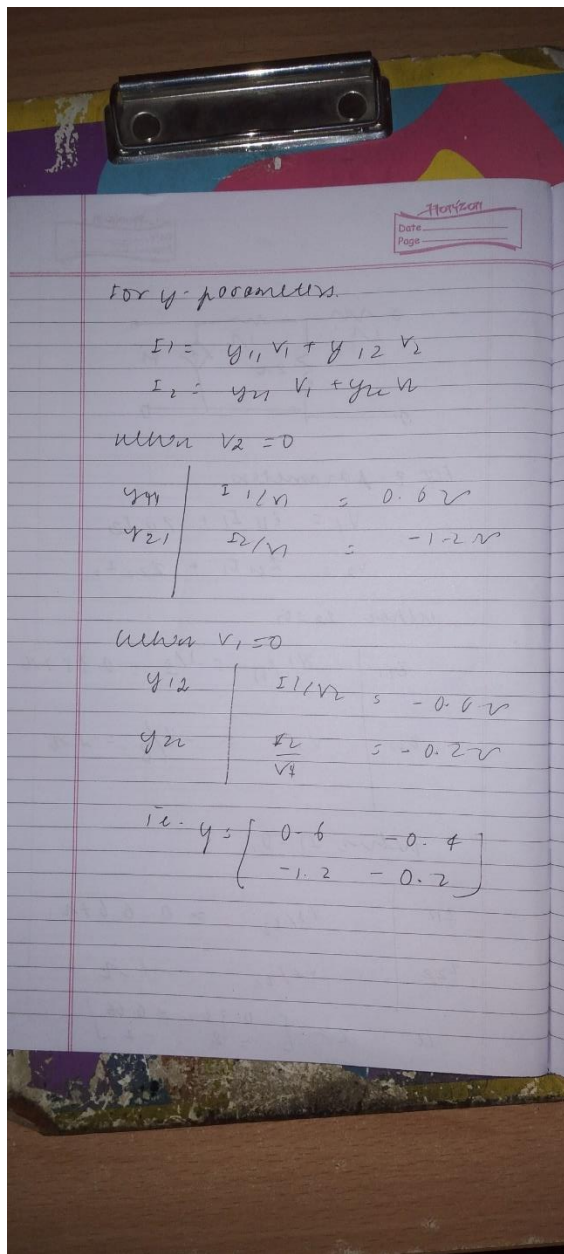


QUCS solution:

a. z-parameters

When I2 is zero (open circuited)

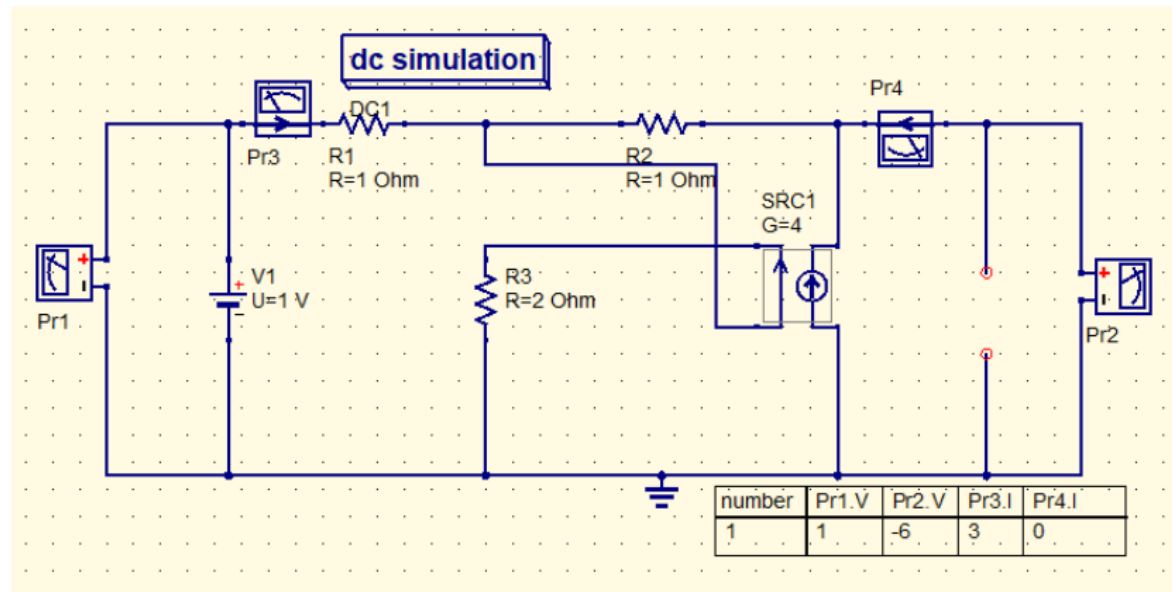


When I1 is zero (open circuited)

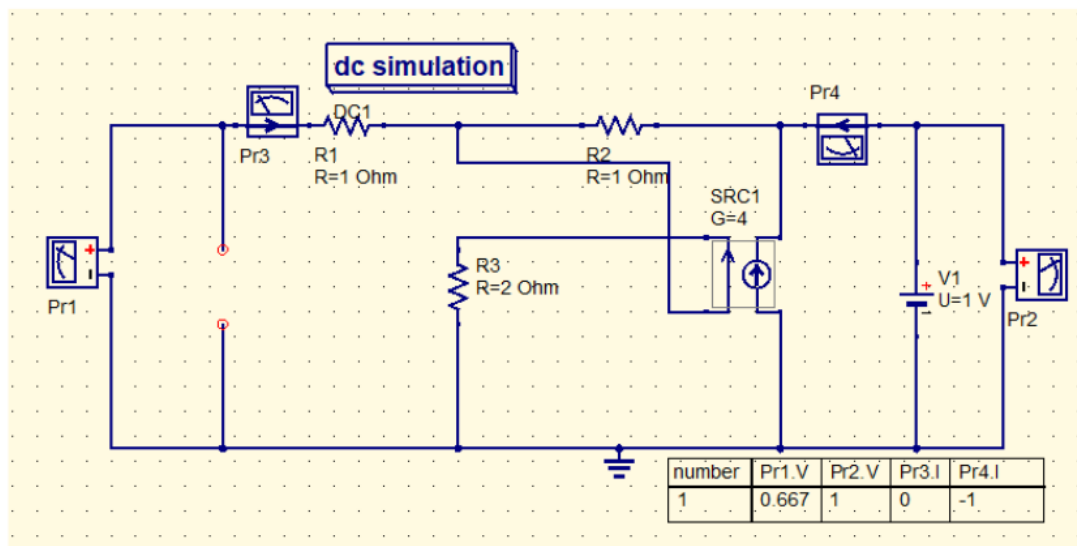


b. h-parameter

When V2 is zero (short circuited)

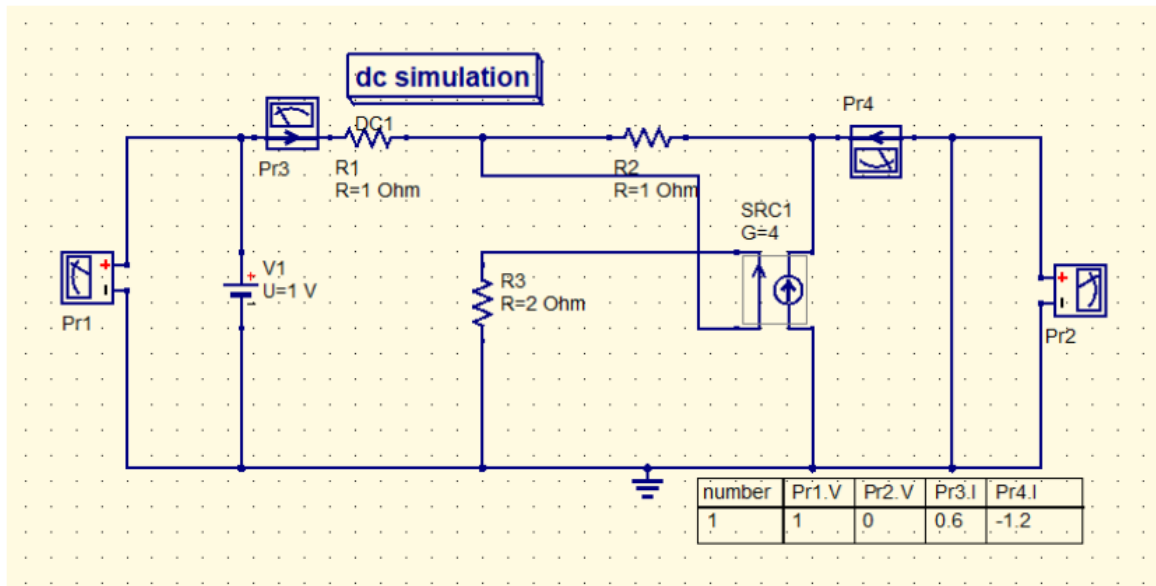


When I1 is zero (open circuited)

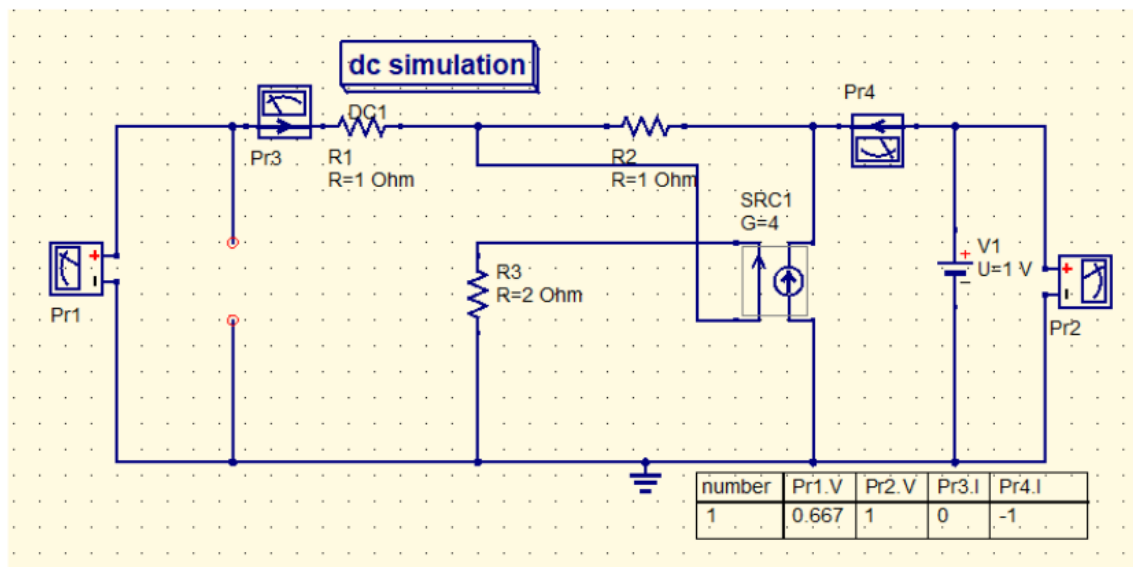


c. T-parameters

When V2 is zero (short circuited)

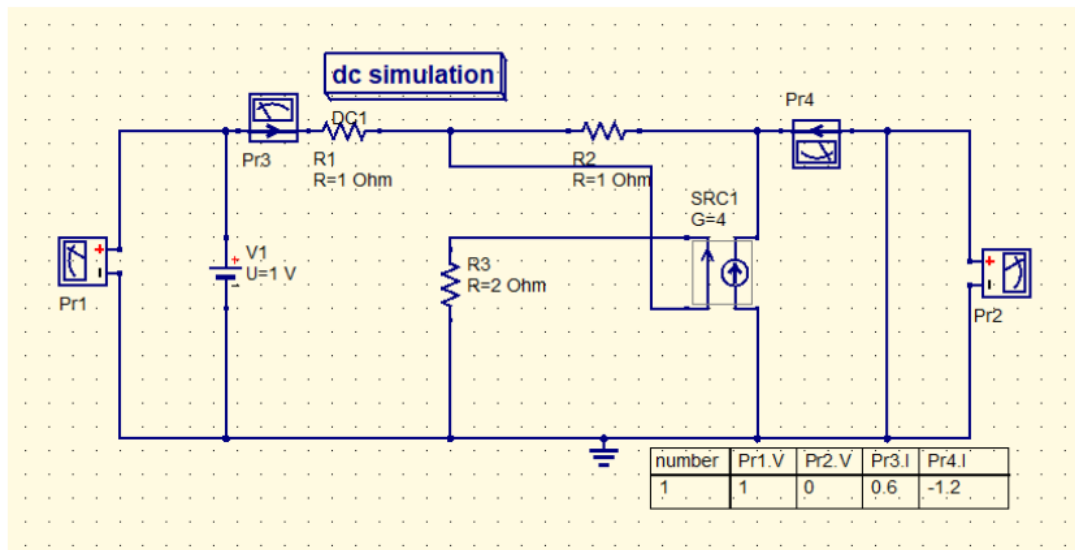


When I2 is zero (open circuited)

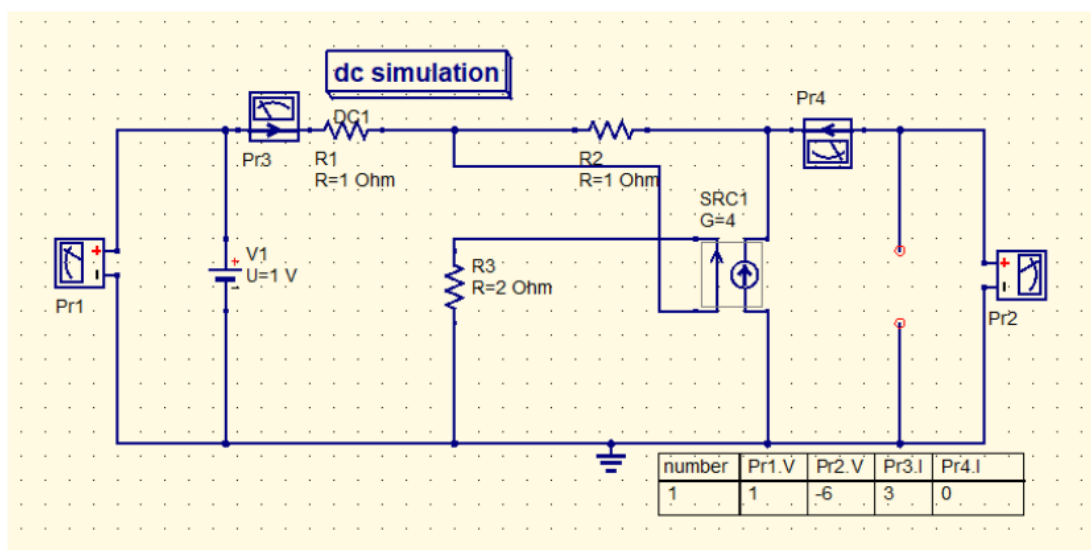

d. y-parameters

When V1 is zero (short circuited)

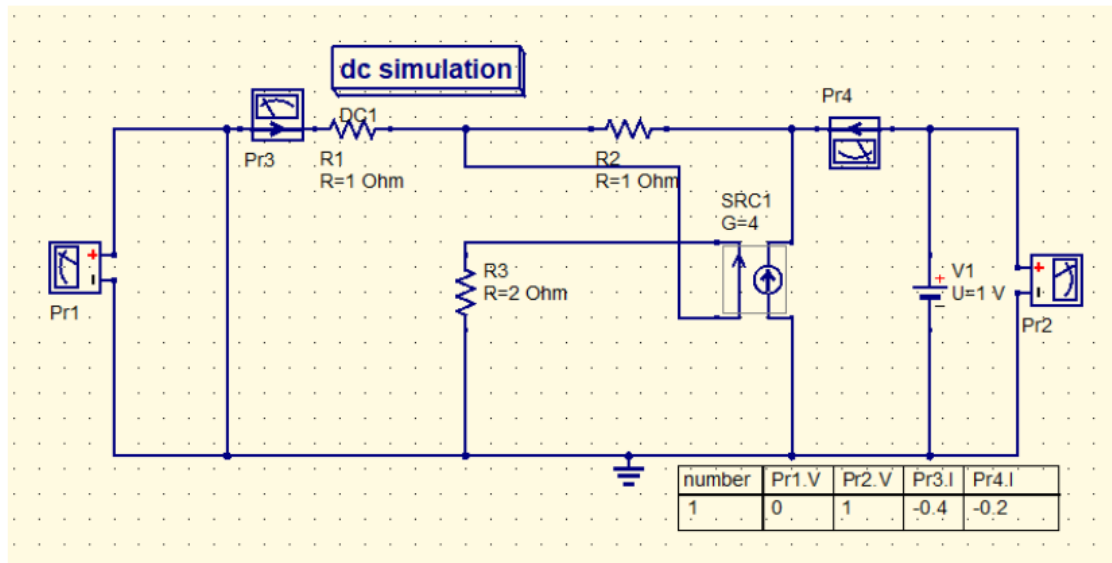

When V2 is zero (short circuited)

